

Transmission Line Types

Lossy Tx Line

$$\begin{aligned}\gamma &= \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)} \\ &= \sqrt{(RG - \omega^2 LC) + j\omega(LG + RC)}\end{aligned}$$

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}} = R_0 + jX_0$$

Lossless Tx Line ($R=G=0$)

* Conductors are perfect and
dielectric medium separates conductors } $\rightarrow Z_0 \rightarrow \infty$


$$\begin{aligned}\gamma &= \alpha + j\beta = \sqrt{(0 + j\omega L)(0 + j\omega C)} \\ &= \sqrt{j^2 \omega^2 LC} \\ &= j\omega \sqrt{LC}\end{aligned}$$

$$\alpha = 0 \quad \text{and} \quad \beta = \omega \sqrt{LC}$$

$$u = \frac{\omega}{\beta} = \frac{\cancel{\omega}}{\cancel{\omega} \sqrt{LC}} = \frac{1}{\sqrt{LC}} = f\lambda$$

$$Z_0 = \sqrt{\frac{0 + j\omega L}{0 + j\omega C}} = \sqrt{\frac{L}{C}} = R_0$$

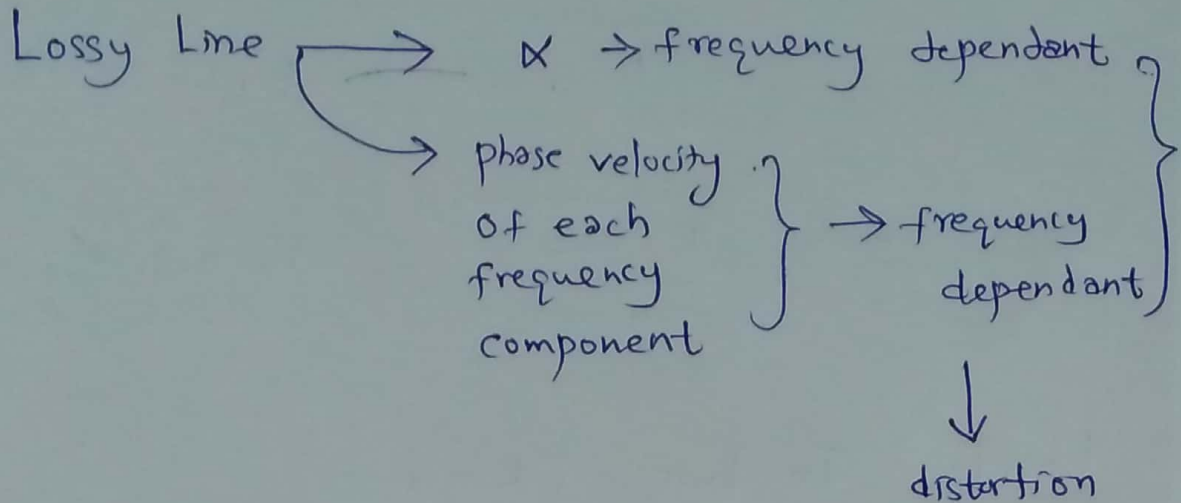Distortionless Tx Line $\left(\frac{R}{L} = \frac{G}{C} \right)$



Distortionless Line $\rightarrow \alpha \rightarrow$ frequency independant

and

$\beta \rightarrow$ linearly depends on the frequency

$$\begin{aligned} \gamma &= \sqrt{(R + j\omega L)(G + j\omega C)} \\ &= \sqrt{RG \left(1 + j\omega \frac{L}{R}\right) \left(1 + j\omega \frac{C}{G}\right)} \\ &= \sqrt{RG \left(1 + j\omega \frac{C}{G}\right) \left(1 + j\omega \frac{C}{G}\right)} \\ &= \sqrt{RG} \left(1 + j\omega \frac{C}{G}\right) \end{aligned}$$

$$\alpha + j\beta = \sqrt{RG} + j\omega \sqrt{RG} \cdot \frac{C}{G}$$

$$= \sqrt{RG} + j\omega \sqrt{\frac{R}{G}} \cdot C$$

$$= \sqrt{RG} + j\omega \sqrt{\frac{L}{C}} \cdot C$$

$$= \sqrt{RG} + j\omega \sqrt{LC}$$

↑

α

↑

β

(not frequency dependant)

$$Z_0 = \sqrt{\frac{R}{G} \frac{(1+j\omega L/R)}{(1+j\omega C/G)}} = \sqrt{\frac{R}{G}} = \sqrt{\frac{L}{C}} = R_0$$

case	$\gamma = \alpha + j\beta$	$Z_0 = R_0 + jX_0$
Lossy	$\sqrt{(R+j\omega L)(G+j\omega C)}$	$\sqrt{\frac{R+j\omega L}{G+j\omega C}}$
Lossless	$0 + j\omega \sqrt{LC}$	$\sqrt{\frac{L}{C}} + j0$
Distortionless	$\sqrt{RC} + j\omega \sqrt{LC}$	$\sqrt{\frac{L}{C}} + j0$

Example

A ^{distortionless} tx line operates at 100 MHz has $Z_0 = 60 \Omega$,
 $\alpha = 20 \text{ mNp/m}$, $u = 0.6c$. Determine
the parameters R, L, G and λ .

Here $c = 3 \times 10^8 \text{ m/s}$,

$$\alpha = \sqrt{RG} = \sqrt{R \cdot \frac{RC}{L}} = R \sqrt{\frac{C}{L}}$$

$$Z_0 = \sqrt{\frac{L}{C}}$$

$$\alpha = \frac{R}{Z_0}$$

$$R = \alpha \cdot Z_0 = (20 \times 10^{-3}) \times 60 = \underline{\underline{1.2 \Omega/\text{m}}}$$

$$\frac{\omega}{\beta} = u = \frac{1}{\sqrt{LC}} \rightarrow L = \frac{Z_0}{u} = \frac{60}{0.6 \times (3 \times 10^8)} = \underline{\underline{333 \text{ nH/m}}}$$

$$G = \frac{\alpha^2}{R} = \frac{(20 \times 10^{-3})^2}{1.2} = \underline{\underline{333 \mu\text{S/m}}}$$

$$u = \frac{1}{\sqrt{LC}} \rightarrow u \cdot \sqrt{\frac{L}{C}} = \frac{1}{C} \rightarrow u Z_0 = \frac{1}{C}$$

$$C = \frac{1}{0.6 \times (3 \times 10^8) \times 60} = \underline{\underline{92.59 \text{ pF/m}}}$$

$$\lambda = \frac{u}{f} = \frac{0.6 \times (3 \times 10^8)}{100 \times 10^6} = \underline{\underline{1.8 \text{ m}}}$$